

# Comparator

Comparators compare two voltages and output “high” or “low” based on which voltage is higher. A slightly modified version of the op-amp assumptions apply:



$$i_+ = i_- = 0 \quad v_+ > v_- \rightarrow v_{OUT} = V_{DD} \quad v_+ < v_- \rightarrow v_{OUT} = V_{SS}$$

Note the following:

- The assumption  $v_+ = v_-$  is no longer true because the circuit is not in negative feedback.
- There are only two possible values for the output voltage  $v_{OUT}$ :  $V_{DD}$  and  $V_{SS}$ .

## Solving comparator problems

When solving comparator problems, you have to essentially solve the circuit for each possible state. Luckily, there are only two possible states:

- $v_{OUT} = V_{DD}$
- $v_{OUT} = V_{SS}$

For a comparator in positive feedback,

- The voltage at the positive input terminal  $v_+$  is determined purely by the output voltage.
- The voltage at the negative input terminal  $v_-$  is determined by the input voltage.

Let's look at this specific example:



No matter the state of the circuit, this relation is true due to the voltage divider relation:

$$v_+ = \frac{R_2}{R_1 + R_2} v_{OUT}$$

And the negative terminal voltage is simply equal to the input voltage:

$$v_- = v_{IN}$$

Let's first look at the case where  $v_- < v_+$ , so  $v_{OUT} = V$ . In this case,

$$v_+ = \frac{R_2}{R_1 + R_2} V$$

This means that this circuit will stay in this state as long as  $v_- < \frac{R_2}{R_1 + R_2} V$ . If  $v_-$  crosses the threshold  $\frac{R_2}{R_1 + R_2} V$ , the output of the circuit will change to  $v_{OUT} = -V$ .

Let's now look at the other case, where  $v_- > v_+$ , so  $v_{OUT} = -V$ . In this case,

$$v_+ = \frac{R_2}{R_1 + R_2} (-V) = -\frac{R_2}{R_1 + R_2} V$$

This means that this circuit will stay in this state as long as  $v_- > -\frac{R_2}{R_1 + R_2} V$ . If  $v_-$  crosses the threshold  $-\frac{R_2}{R_1 + R_2} V$ , the output of the circuit will change to  $v_{OUT} = V$ .

To summarize the results, if  $v_{OUT} = V$ , for  $v_{OUT}$  to transition to  $-V$ ,  $v_{in}$  has to become greater than  $\frac{R_2}{R_1 + R_2} V$ . And if  $v_{OUT} = -V$ , for  $v_{OUT}$  to transition to  $V$ ,  $v_{in}$  has to become less than  $-\frac{R_2}{R_1 + R_2} V$ . Notice that the threshold for the input voltage changes depending on the current output voltage. This gives us hysteresis.

Let's plot the transfer curve (output voltage as a function of input voltage) of this behavior.



Notice the arrows on the inner rectangle. They signify that to go from a high output to low output, the input must cross  $\frac{R_2}{R_1 + R_2} V$ , whereas to go from a low output to a high output, the input must cross  $-\frac{R_2}{R_1 + R_2} V$ .

What if we apply a triangle wave to the input?



From:

<https://www.jaeyoung.wiki/> - Jaeyoung Wiki

Permanent link:

<https://www.jaeyoung.wiki/kb:comparator>

Last update: **2024-04-30 04:03**