

Time-averaging circuit variables

Finding the time average of circuit variables is commonly done in power electronics. It is usually very difficult to calculate time averages explicitly by finding time-varying expressions for the variable in questions and integrating. Instead, we can use the constitutive relations of capacitors and/or inductors to greatly simplify the math.

Recall the constitutive relations of capacitors and inductors:

$$i_C(t) = C \frac{dv_C}{dt} \quad v_L(t) = L \frac{di_L}{dt}$$

Let's assume that whatever circuit we're working with is in cyclic steady state. (This is usually given.) Then, what happens when we calculate the time average of $i_C(t)$ over a single period from $t = 0$ to $t = T$?

$$\langle i_C \rangle = \frac{1}{T} \int_0^T i_C(t) dt = \frac{1}{T} \int_0^T C \frac{dv_C}{dt} dt = \frac{1}{T} C(v_C(T) - v_C(0)) = 0$$

Because we assumed that the circuit is in cyclic steady state, $v_C(T) = v_C(0)$. (More generally, $v_C(t + T) = v_C(t)$.)

We can do similar math to find the time average of $v_L(t)$ over a single period:

$$\langle v_L \rangle = \frac{1}{T} \int_0^T v_L(t) dt = \frac{1}{T} \int_0^T L \frac{di_L}{dt} dt = \frac{1}{T} L(i_L(T) - i_L(0)) = 0$$

So now we know, that in cyclic steady state,

$$\langle i_C \rangle = 0 \quad \langle v_L \rangle = 0$$

How do we use these relations to solve for the time average of other circuit variables? Let's look at an example.

Example (from Fall 2018 Quiz 2 Problem 2)

Consider the following RL circuit. A square wave voltage with period 40ms and duty cycle 50% is applied. Numerically determine the average value of the current i_m in the cyclic steady state.



The problem is asking for the time average of $i_m(t)$. We could solve for $\langle i_m \rangle$ by solving for $\langle v_R \rangle$ and dividing by R_m (Ohm's law). How can we find $\langle v_m \rangle$? Let's write out the KVL equation for this circuit:

$$v_{IN}(t) - v_L(t) - v_R(t) = 0$$

$$v_R(t) = v_{IN}(t) - v_L(t)$$

We can take the time average of each term in this equation, and the resulting equation will still be valid (because time-averaging is a linear operation):

$$\langle v_R \rangle = \langle v_{IN} \rangle - \langle v_L \rangle$$

And as we found above, $\langle v_L \rangle = 0$.

$$\langle v_R \rangle = \langle v_{IN} \rangle - 0 = \langle v_{IN} \rangle$$

$$\langle v_{IN} \rangle = 5V \times 50\% = 2.5V$$

$$\langle i_m \rangle = \frac{2.5V}{R}$$

Much easier than integrating a bunch of exponential decay functions.

From:

<https://www.jaeyoung.wiki/> - **Jaeyoung Wiki**

Permanent link:

https://www.jaeyoung.wiki/kb:time_averaging

Last update: **2024-04-30 04:03**